

Last name:	First name:	Group:	Mark: / 20
------------	-------------	--------	---------------

Electronic Fundamentals Exam

Exercise 1 (6pts)

Consider the circuit presented in **Figure 1**. A load resistor R_4 is connected between the output terminals **A** and **B**.

Given: $E_1 = 4\text{ V}$, $R_1 = 16\ \Omega$, $R_2 = 4\ \Omega$, $R_3 = 6\ \Omega$, and $R_4 = 24\ \Omega$.

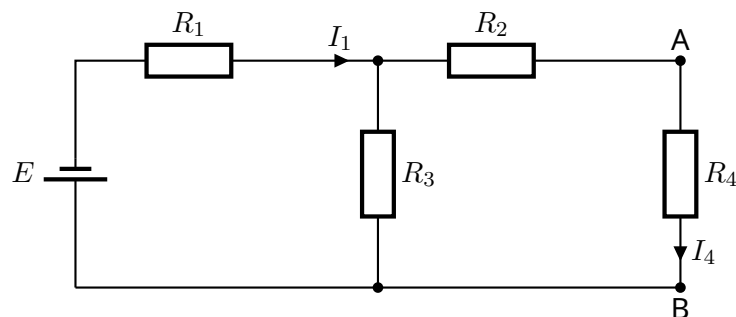


Figure 1

- Determine the expression and calculate the equivalent resistance R_{eq} as a function of R_1 , R_2 , R_3 and R_4
.....
.....
- Calculate the current I_1 using Kirchhoff's Voltage Law (loop law).
.....
- Using Figure 1 and applying Norton's theorem, determine the expression of the Norton current I_N in terms of I_1 , R_2 , and R_3 as seen across the load resistor R_4
.....
.....
- Calculate the value of the Norton current I_N
.....

5. Give the expression of Norton resistance R_N and calculate its numerical value.

.....

Exercise 2 (5pts)

- Four options are provided as possible answers to the following questions. each question has only ONE correct answer. Choose the correct answer and write the letter (A-D) next to the question.

Consider the circuit shown in **Figure 2**. The diodes D_1 and D_2 are ideal diodes. The input voltage is:

$$e(t) = 100\sqrt{2}\sin(100\pi t)$$

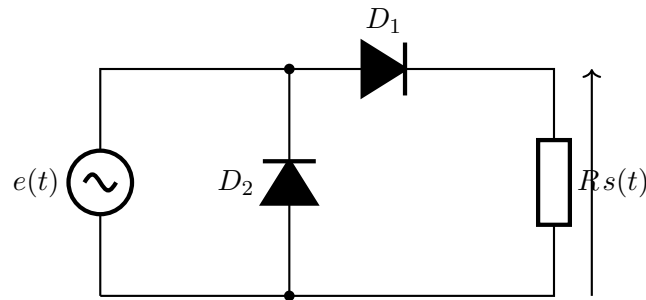


Figure 2

1. When $e(t) > 0$, the diodes are:

☐

- A. D_1 conducting and D_2 blocked
B. D_1 blocked and D_2 conducting

- C. Both diodes conducting
D. Both diodes blocked

2. When $e(t) < 0$, the diodes are:

☐

- A. D_1 conducting and D_2 blocked
B. D_1 blocked and D_2 conducting

- C. Both diodes conducting
D. Both diodes blocked

3. The output voltage $s(t)$ is equal to:

☐

- A. $e(t)$ for all values of t
B. 0 for all values of t

- C. $e(t)$ when $e(t) > 0$, and 0 when $e(t) < 0$
D. $-e(t)$ when $e(t) > 0$

4. For $t = \frac{1}{400}$ s, determine the value of the resistance R if the effective current through the resistor is equal to 10 mA.

☐

- A. 1 k Ω
B. 5 k Ω

- C. 10 k Ω
D. 51 k Ω

5. The maximum current through R is:

☐





A. 14.14 mA

C. 20.20 mA

B. 11.11 mA


D. 19.19 mA

6. The output signal $s(t)$ is shown below. Which graph correctly represents $s(t)$?

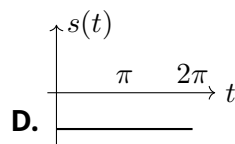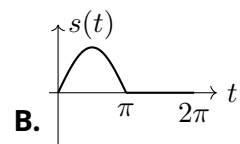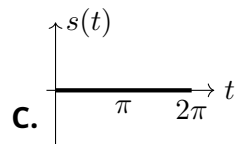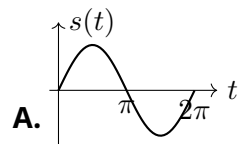☐

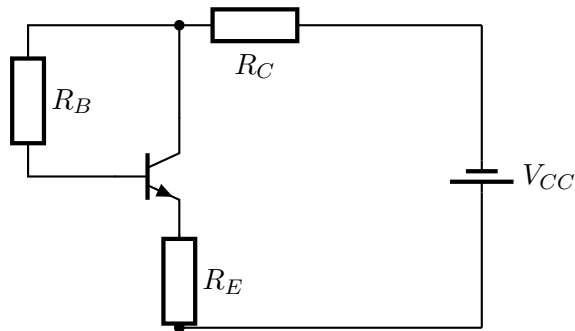Exercise 3 (9pts)

A silicon NPN transistor is biased using a resistor connected between the collector and the base, as shown in the diagram.



1. On the circuit diagram, identify the transistor terminals: base (B), collector (C), and emitter (E).
2. Indicate on the diagram the directions of the voltages V_{CE} , V_{CB} , and V_{BE} .
3. Show on the circuit diagram the directions of the currents I_B , I_C , and I_E .
4. Give the relationships between these three currents (I_B , I_C , and I_E).
5. Establish the equation of the DC load line $I_C = f(V_{CE})$ (output characteristic).

6. Determine the saturation current I_{Csat} corresponding to the condition $V_{CE} = 0V$

.....

7. Determine the cutoff voltage V_{CE} corresponding to the condition $I_C = 0A$

.....

8. Establish the equation of the input line $I_B = f(V_{BE})$ (input characteristic).

.....

.....

9. Plot the DC load line $I_C = f(V_{CE})$ (output characteristic).

.....

.....

.....

.....

.....

10. Calculate the values of I_C and I_B required so that $V_{CE} = 5V$, while keeping the other parameters unchanged.

.....

.....

.....

Given:

$\beta = 65$, $V_{CC} = 10V$, $V_{BE} = 0.7V$, $R_B = 17\text{ k}\Omega$, $R_C = 1\text{ k}\Omega$, and $R_E = 100\text{ }\Omega$.