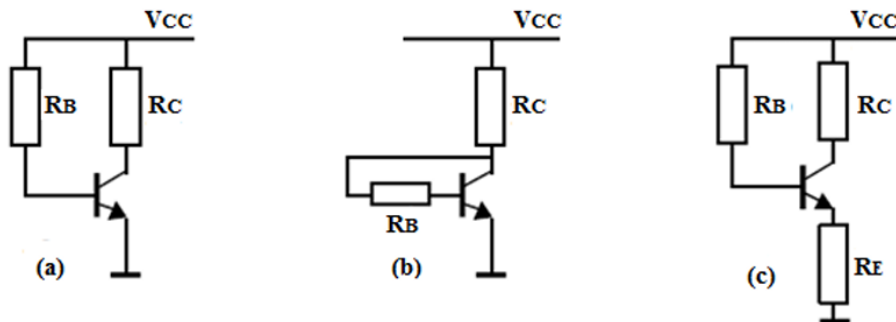


Exercise Series 3 Bipolar Transistor

Exercise 1 (course)

Consider the transistor biasing circuits shown below. The given data are: $V_{CC}=15V$, $V_{BE}=0.7 V$, $R_C=1K\Omega$, $R_B=220 K\Omega$, $R_E=110 \Omega$.



- For each of the three configurations, calculate the current I_C for $\beta = 100$ and then for $\beta = 300$.
- Which configuration is the least sensitive to variations in β ?


Exercise 2

The figure below represents a **biasing circuit of an NPN transistor** using two base resistors.

Given:

$\beta = 15$, $V_{BE} = 0.7 V$, $R_1 = 6.8 k\Omega$, $R_2 = 2.2 k\Omega$, $R_C = 3 k\Omega$, and $R_E = 2 k\Omega$.

- Transform the biasing circuit seen from the **base of the transistor** into its **Thevenin equivalent**, and calculate V_{TH} and R_{TH} .
- Calculate the collector current I_C for $\beta = 100$ and $\beta = 300$. Draw a conclusion.

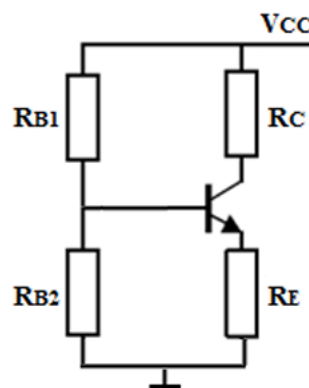


Exercise 3

Using Kirchhoff's law (node law), find the expression relating:
 V_{BE} , I_B , U_o , R_a , and R_B .

2/ Find the same expression using **Thevenin's theorem** applied between points **B** and **M**.

3/ Determine the operating point (Q point)
(at the middle of the DC load line)

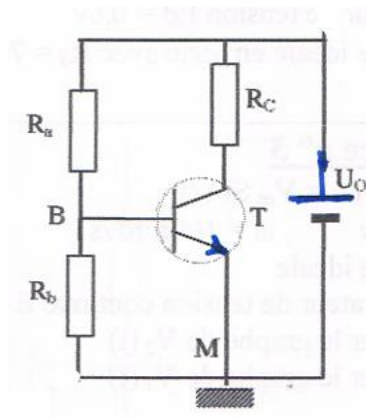given: $U_o = 10\text{ V}$, $V_{BE} = 0.6\text{ V}$, $I_B = 35\text{ }\mu\text{A}$, $R_C = 1\text{ k}\Omega$, $R_a = 200\text{ k}\Omega$, $R_b = 50\text{ k}\Omega$.




Exercise 4 (course)

A silicon **NPN transistor** is biased using a **voltage-divider base bias circuit**, as shown in the figure opposite.

Given: $\beta = 100$ and $V_{CC} = 10\text{ V}$.


The desired operating point is characterized by:

- $V_{CE0} = 5\text{ V}$, $I_{C0} = 1\text{ mA}$ and $V_{BE0} = 0.7\text{ V}$
1. Determine the **Thevenin equivalent circuit** between the transistor base and ground.
 2. Deduce the equation of the **static input line**.
 3. If R_{B1} must be ten times greater than R_{B2} , calculate the values of R_{B1} and R_{B2} .
 4. Derive the equation of the **static load line**.
 5. Calculate the value of the collector resistor R_C .

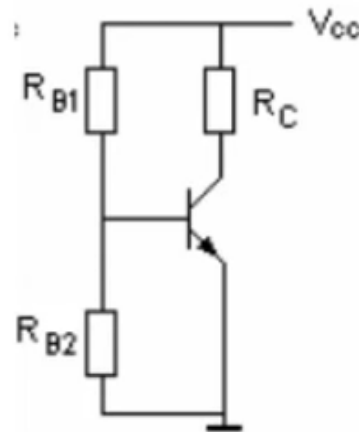

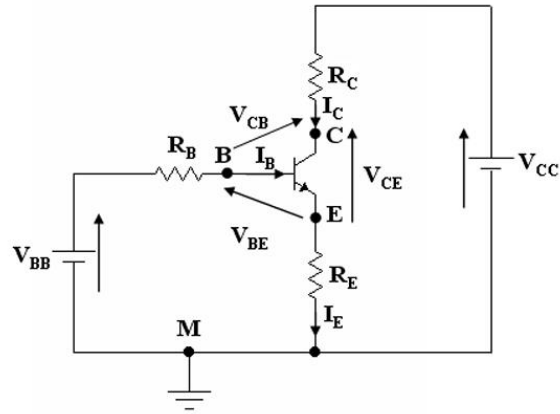Exercise 5

Consider the circuit shown in the following figure:



1. Calculate the operating point values (I_B , I_C , and V_{CE}).
2. Derive and plot the equations of the lines: $I_C = f(V_{CE})$ and $I_B = f(V_{BE})$.
3. Represent the operating point on its corresponding lines.

Given data:

$\beta = 180$, $V_{BB} = 5 \text{ V}$, $V_{CC} = 10 \text{ V}$, $V_{BE} = 0.6 \text{ V}$, $R_B = 10 \text{ k}\Omega$, and $R_C = R_E = 100 \text{ }\Omega$.